

# Developmental Testing for Opamp Circuits

By Nolan Manteufel with ChatGPT

When designing and testing operational amplifier (op-amp) amplifier circuits, it's essential to verify their functionality and performance. Here are some common developmental tests and measurements you can perform:

## DC Biasing Test:

Measure and verify the DC voltage levels at the input and output terminals to ensure proper biasing.

Check that the DC offset at the output is within an acceptable range.

## AC Gain Measurement:

Apply an AC signal at the input (typically a sinusoidal waveform) and measure the output AC voltage.

Calculate the voltage gain ( $A_v$ ) as the ratio of output voltage to input voltage ( $A_v = V_{out} / V_{in}$ ).

## Frequency Response:

Sweep the input signal frequency over a range of interest (e.g., low-frequency audio, high-frequency RF).

Measure the voltage gain at different frequencies to assess the bandwidth and frequency response of the circuit.

**Input and Output Impedance:**

Measure the input impedance of the circuit by applying a test signal through a known source impedance and observing the voltage drop.

Measure the output impedance by connecting a load resistor and measuring the voltage drop as the load resistor value changes.

**Distortion and Linearity:**

Apply a sine wave input and check for harmonic distortion in the output signal using a spectrum analyzer.

Ensure the circuit operates linearly within the specified input range.

**Common-Mode Rejection Ratio (CMRR):**

Apply a common-mode signal (identical voltage applied to both inputs) and measure the output.

Calculate the CMRR as the ratio of the differential gain to the common-mode gain.  $CMRR = A_d / A_{cm}$ .

**Slew Rate:**

Apply a step input signal (fast transition) and measure the rate at which the output voltage changes.

The slew rate is the maximum rate of change in the output voltage and is crucial in applications requiring fast signal processing.

**Noise and Signal-to-Noise Ratio (SNR):**

Measure the output noise level in the absence of an input signal using an oscilloscope or spectrum analyzer.

Calculate the SNR as the ratio of the signal amplitude to the noise level.

**Input and Output Offset Voltage:**

Measure the input offset voltage by shorting the inputs and measuring the resulting output voltage.

Measure the output offset voltage by applying a known input voltage and measuring the deviation from the expected output.

**Transient Response:**

Apply a step input and measure the time it takes for the output to reach a stable state.

Assess the rise time, settling time, and overshoot.

**Temperature Stability:**

Test the circuit over a range of temperatures to evaluate its performance under different thermal conditions.

Check for variations in gain, offset, and other parameters.

**Power Supply Sensitivity:**

Vary the power supply voltage within its specified range and measure the effect on the circuit's performance.

Assess how sensitive the circuit is to supply voltage fluctuations.

**PSRR (Power Supply Rejection Ratio):**

Apply a known AC signal to the power supply and measure the output response.

Calculate the PSRR as the ratio of the change in output voltage to the change in supply voltage.

**Input and Output Limitations:**

Determine the maximum allowable input voltage that does not cause clipping or distortion.

Measure the output voltage range before clipping occurs.

When conducting these tests, ensure you follow proper safety guidelines and use appropriate measurement equipment, including oscilloscopes, multimeters, signal generators, and spectrum analyzers. Additionally, refer to the datasheet of the specific op-amp you are using for recommended test conditions and performance specifications.

## Change and Liability Notice

This document is subject to change without notice. While effort has been made to ensure the accuracy of the material contained within this document, Nolan Manteufel shall under no circumstances be liable for incidental or consequential damages or related expenses resulting from the use of this document.

## Trademark Notice

miniPCB is a trademark of Nolan Manteufel. This document does not constitute permission to use the miniPCB trademark.

WORDMARK	FIGUREMARK	FIGUREMARK
miniPCB™		

## Revision History

REV	DESCRIPTION	ECO	DATE
A	Initial Release	N/A	08NOV2023